

PHYS 230 - Electricity and Magnetism

Lecture 18

Instructor: Saeed Rastgoo



**UNIVERSITY
OF ALBERTA**

Outline

4 Capacitance and Dielectrics

- Capacitors in Series vs. Parallel Connection
- Energy Stored in a Capacitor

All figures in these slides are from one of the following sources, unless cited otherwise:

University Physics With Modern Physics, Young & Freedman

Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett

Outline

4 Capacitance and Dielectrics

- Capacitors in Series vs. Parallel Connection
- Energy Stored in a Capacitor

All figures in these slides are from one of the following sources, unless cited otherwise:


University Physics With Modern Physics, Young & Freedman

Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett

Series Connection and Equivalent Capacitance

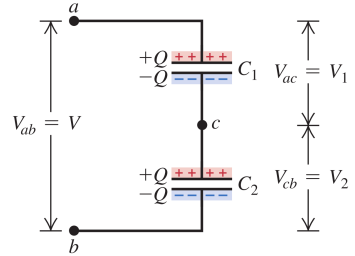
For capacitors in **series** connection we have



Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have


$$\left\{ Q_1 = Q_2 \right.$$

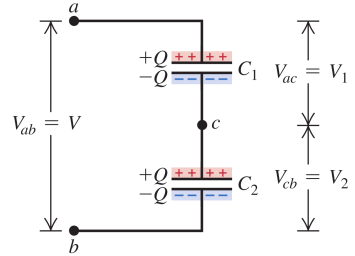

Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have


$$\left\{ Q_1 = Q_2 = Q \right.$$

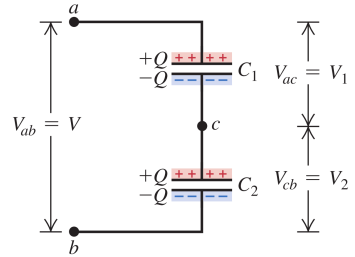

Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

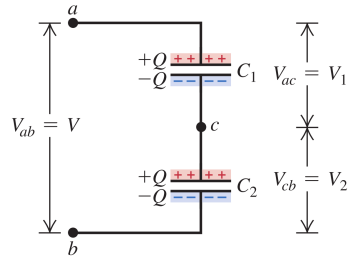
$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} \end{cases}$$



Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have
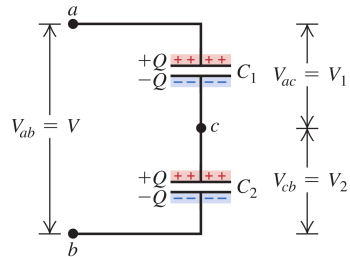
$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$




Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

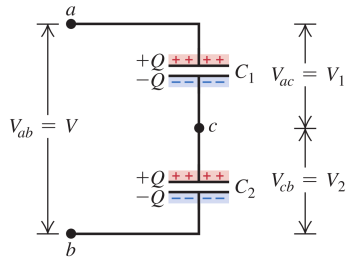because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$




Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

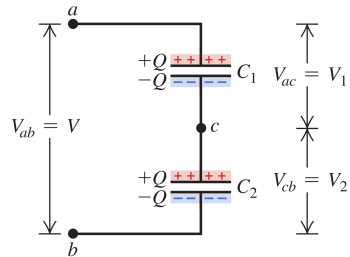because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write




Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write

$$V_1 + V_2 = V$$

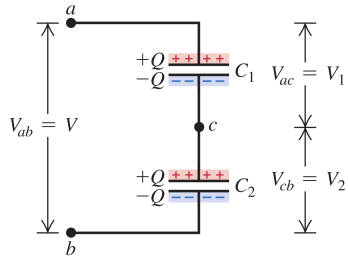


Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write
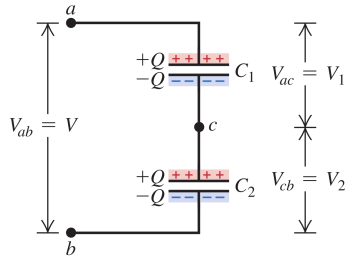
$$V_1 + V_2 = V \Rightarrow \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V$$




Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write
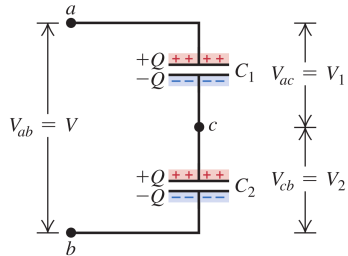
$$V_1 + V_2 = V \Rightarrow \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V \Rightarrow \frac{Q}{C_1} + \frac{Q}{C_2} = V$$




Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have

$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write
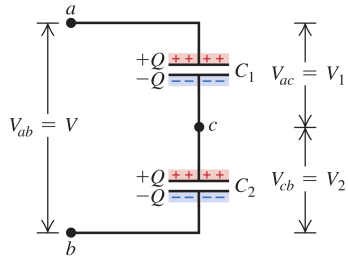
$$V_1 + V_2 = V \Rightarrow \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V \Rightarrow \frac{Q}{C_1} + \frac{Q}{C_2} = V \Rightarrow Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = V$$



Series Connection and Equivalent Capacitance

For capacitors in **series** connection we have


$$\begin{cases} Q_1 = Q_2 = Q \\ V_1 + V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write

$$V_1 + V_2 = V \Rightarrow \frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V \Rightarrow \frac{Q}{C_1} + \frac{Q}{C_2} = V \Rightarrow Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = V$$

and hence

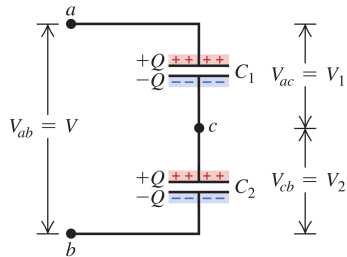
$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$



Series Connection and Equivalent Capacitance

The RHS of the equation
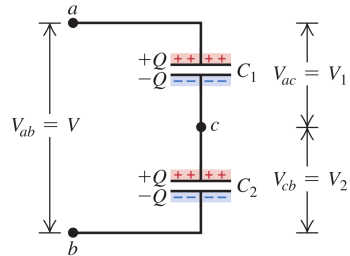
$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$




Series Connection and Equivalent Capacitance

The RHS of the equation

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$

is the “series equivalent potential” of a single device with

$$V = V_1 + V_2$$

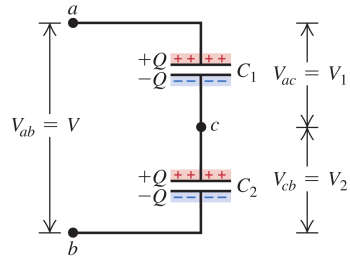

Series Connection and Equivalent Capacitance

The RHS of the equation


$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$

is the “series equivalent potential” of a single device with

$$V = V_1 + V_2$$

divided by the “series equivalent charge” of the single device

$$Q = Q_1 = Q_2$$

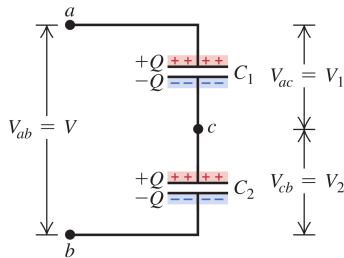

Series Connection and Equivalent Capacitance

The RHS of the equation

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$

is the “series equivalent potential” of a single device with


$$V = V_1 + V_2$$

divided by the “series equivalent charge” of the single device

$$Q = Q_1 = Q_2$$

Hence it is the inverse of “series equivalent capacitance” of the single device C
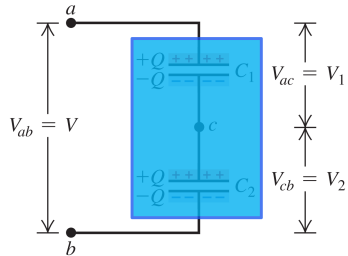
$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C}$$



Series Connection and Equivalent Capacitance

The RHS of the equation

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{V}{Q}$$

is the “series equivalent potential” of a single device with



$$V = V_1 + V_2$$

divided by the “series equivalent charge” of the single device

$$Q = Q_1 = Q_2$$

Hence it is the inverse of “series equivalent capacitance” of the single device C
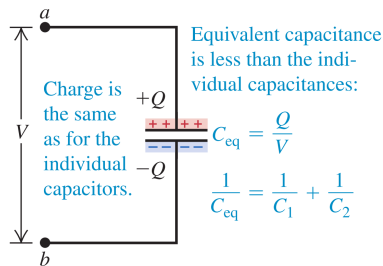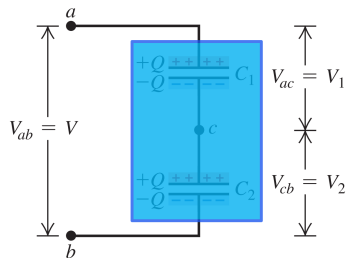
$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C}$$



Series Connection and Equivalent Capacitance

Two capacitors with capacitance C_1 and C_2 connected in series are equivalent to a single capacitor with

- the same charge

$$Q = Q_1 = Q_2$$

- potential difference

$$V = V_1 + V_2$$


- capacitance

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C = \frac{C_1 C_2}{C_1 + C_2}$$

is always smaller than the individual capacitances

Parallel Connection and Equivalent Capacitance

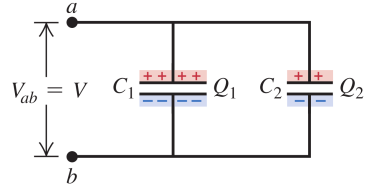
For capacitors in **parallel** connection we have



Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

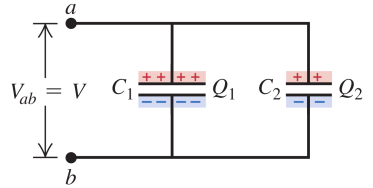
$$\left\{ \begin{array}{l} Q_1 + Q_2 = Q \end{array} \right.$$



Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

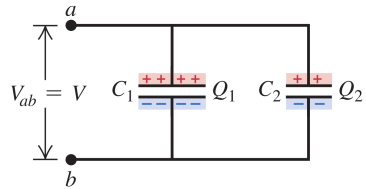
$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} \end{cases}$$



Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have
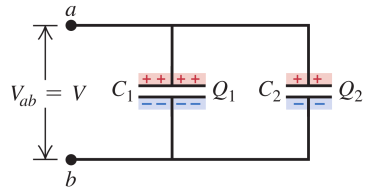
$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$




Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

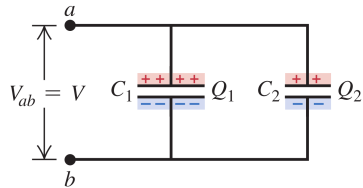because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$




Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

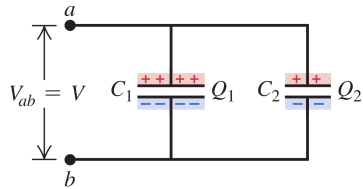because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write




Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write

$$Q_1 + Q_2 = Q$$

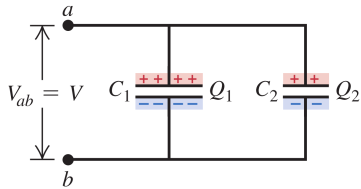


Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write
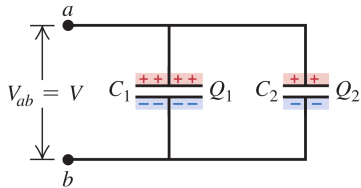
$$Q_1 + Q_2 = Q \Rightarrow C_1 V_1 + C_2 V_2 = Q$$




Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write
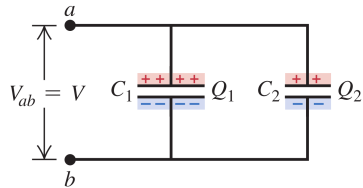
$$Q_1 + Q_2 = Q \Rightarrow C_1 V_1 + C_2 V_2 = Q \Rightarrow C_1 V + C_2 V = Q$$




Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have

$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$

because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write

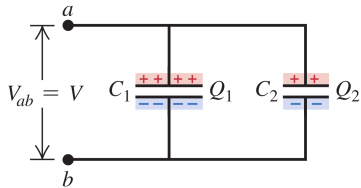
$$Q_1 + Q_2 = Q \Rightarrow C_1 V_1 + C_2 V_2 = Q \Rightarrow C_1 V + C_2 V = Q \Rightarrow V(C_1 + C_2) = Q$$



Parallel Connection and Equivalent Capacitance

For capacitors in **parallel** connection we have
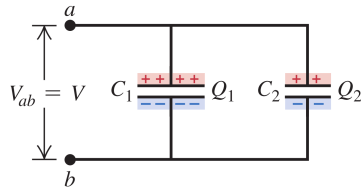
$$\begin{cases} Q_1 + Q_2 = Q \\ V_1 = V_2 = V_{ab} = V \end{cases}$$



because $C_1 = \frac{Q_1}{V_1}$ and $C_2 = \frac{Q_2}{V_2}$ we can write

$$Q_1 + Q_2 = Q \Rightarrow C_1 V_1 + C_2 V_2 = Q \Rightarrow C_1 V + C_2 V = Q \Rightarrow V(C_1 + C_2) = Q$$


and hence

$$C_1 + C_2 = \frac{Q}{V}$$

Parallel Connection and Equivalent Capacitance

The RHS of the equation

$$C_1 + C_2 = \frac{Q}{V}$$

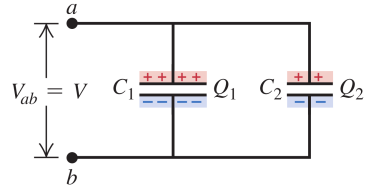


Parallel Connection and Equivalent Capacitance

The RHS of the equation

$$C_1 + C_2 = \frac{Q}{V}$$

is the “parallel equivalent charge” of a single device with

$$Q = Q_1 + Q_2$$

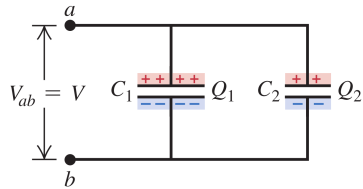

Parallel Connection and Equivalent Capacitance

The RHS of the equation


$$C_1 + C_2 = \frac{Q}{V}$$

is the “parallel equivalent charge” of a single device with

$$Q = Q_1 + Q_2$$

divided by the “parallel equivalent potential” of the single device

$$V = V_1 = V_2$$

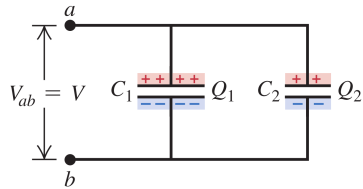

Parallel Connection and Equivalent Capacitance

The RHS of the equation

$$C_1 + C_2 = \frac{Q}{V}$$

is the “parallel equivalent charge” of a single device with


$$Q = Q_1 + Q_2$$

divided by the “parallel equivalent potential” of the single device

$$V = V_1 = V_2$$

Hence it is the “parallel equivalent capacitance” of the single device C

$$C_1 + C_2 = C$$

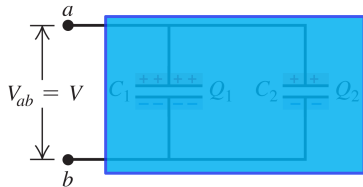

Parallel Connection and Equivalent Capacitance

The RHS of the equation

$$C_1 + C_2 = \frac{Q}{V}$$

is the “parallel equivalent charge” of a single device with



$$Q = Q_1 + Q_2$$

divided by the “parallel equivalent potential” of the single device

$$V = V_1 = V_2$$

Hence it is the “parallel equivalent capacitance” of the single device C

$$C_1 + C_2 = C$$

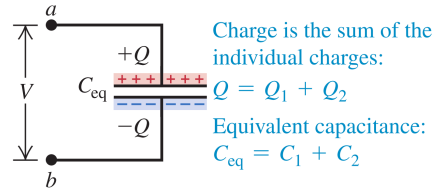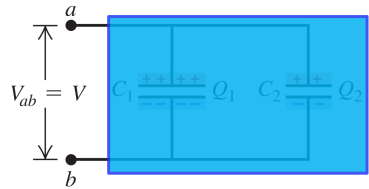

Parallel Connection and Equivalent Capacitance

Two capacitors with capacitance C_1 and C_2 connected in parallel are equivalent to a single capacitor with

- the charge

$$Q = Q_1 + Q_2$$

- the same potential difference

$$V = V_1 = V_2$$

- capacitance


$$C = C_1 + C_2$$

is always larger than the individual capacitances

Exercise I


<https://epoll.srv.ualberta.ca> – Code: MBD

In figure $C_1 = 6\ \mu\text{F}$ and $C_2 = 3\ \mu\text{F}$ and $V_{ab} = 18\ \text{V}$. Find the equivalent capacitance, the charge, and potential difference for each capacitor.

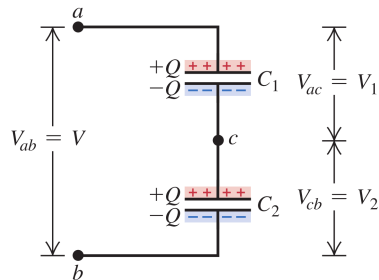

Exercise I


<https://epoll.srv.ualberta.ca> – Code: MBD

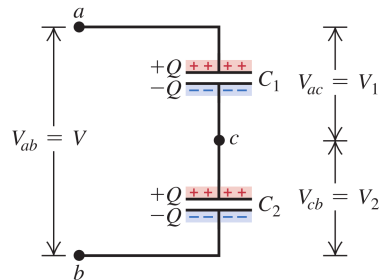

Exercise 2


<https://epoll.srv.ualberta.ca> – Code: MBD

In figure $C_1 = 6 \mu\text{F}$ and $C_2 = 3 \mu\text{F}$ and $V_{ab} = 18 \text{ V}$. Find the equivalent capacitance, the charge, and potential difference for each capacitor.

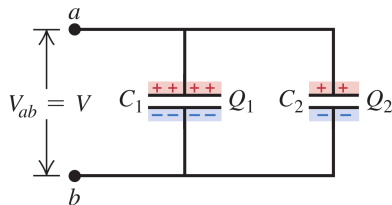

Exercise 2

<https://epoll.srv.ualberta.ca> – Code: MBD

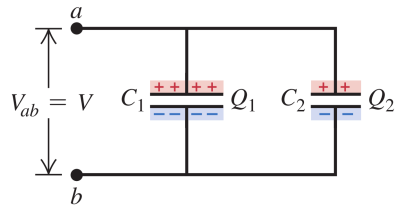


Exercise 3

<https://epoll.srv.ualberta.ca> – Code: MBD

Find the equivalent capacitance of the five-capacitor network shown in figure.


Figure 24.10 (a) A capacitor network between points a and b . (b) The $12\ \mu\text{F}$ and $6\ \mu\text{F}$ capacitors in series in (a) are replaced by an equivalent $4\ \mu\text{F}$ capacitor. (c) The $3\ \mu\text{F}$, $11\ \mu\text{F}$, and $4\ \mu\text{F}$ capacitors in parallel in (b) are replaced by an equivalent $18\ \mu\text{F}$ capacitor. (d) Finally, the $18\ \mu\text{F}$ and $9\ \mu\text{F}$ capacitors in series in (c) are replaced by an equivalent $6\ \mu\text{F}$ capacitor.

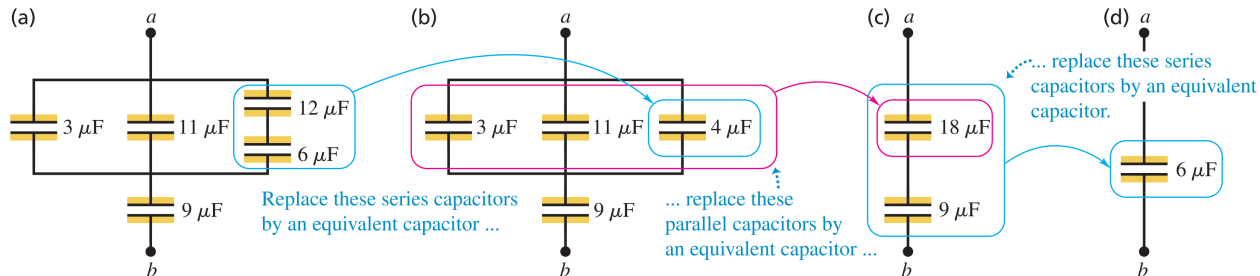

Exercise 3

<https://epoll.srv.ualberta.ca> – Code: MBD

Figure 24.10 (a) A capacitor network between points a and b . (b) The $12\ \mu\text{F}$ and $6\ \mu\text{F}$ capacitors in series in (a) are replaced by an equivalent $4\ \mu\text{F}$ capacitor. (c) The $3\ \mu\text{F}$, $11\ \mu\text{F}$, and $4\ \mu\text{F}$ capacitors in parallel in (b) are replaced by an equivalent $18\ \mu\text{F}$ capacitor. (d) Finally, the $18\ \mu\text{F}$ and $9\ \mu\text{F}$ capacitors in series in (c) are replaced by an equivalent $6\ \mu\text{F}$ capacitor.

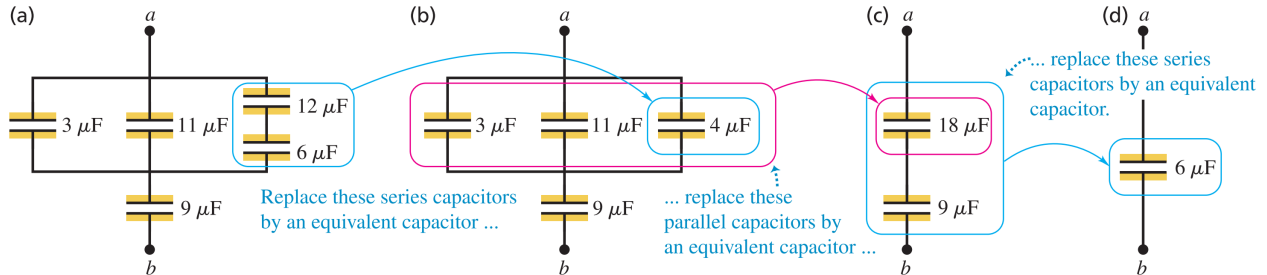

Outline

4 Capacitance and Dielectrics

- Capacitors in Series vs. Parallel Connection
- Energy Stored in a Capacitor

All figures in these slides are from one of the following sources, unless cited otherwise:

University Physics With Modern Physics, Young & Freedman

Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett

Energy Stored in a Capacitor

- Electric potential energy stored in a charged capacitor = amount of work required to charge it
 - i.e., to separate opposite charges and place them on different conductors

Energy Stored in a Capacitor

- Electric potential energy stored in a charged capacitor = amount of work required to charge it
 - i.e., to separate opposite charges and place them on different conductors
- When the capacitor is discharged, this stored energy is recovered as work done by electrical forces

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r} = dq \int_{-}^{+} - \underbrace{\nabla v \cdot d\mathbf{r}}_{dv}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r} = dq \int_{-}^{+} - \underbrace{\nabla v \cdot d\mathbf{r}}_{dv} = -dq \int_{-}^{+} dv$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r} = dq \int_{-}^{+} - \underbrace{\nabla v \cdot d\mathbf{r}}_{dv} = -dq \int_{-}^{+} dv = -vdq$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r} = dq \int_{-}^{+} - \underbrace{\nabla v \cdot d\mathbf{r}}_{dv} = -dq \int_{-}^{+} dv = -vdq$$

and the work done by us is the negative of (or against) the work done by the field

$$dW_{\text{us}} = -dW_{\text{field}}$$

Energy Stored in a Capacitor

When a capacitor is fully charged to Q , and potential difference is V , we have

$$C = \frac{Q}{V}$$

In an intermediate stage of charging with charge $q < Q$ and $v < V$, we have

$$C = \frac{q}{v}$$

At this stage, if a charge dq is moved from the negative plate to the positive plate, the work done by the field is

$$dW_{\text{field}} = \int_{-}^{+} \mathbf{F} \cdot d\mathbf{r} = dq \int_{-}^{+} \mathbf{E} \cdot d\mathbf{r} = dq \int_{-}^{+} - \underbrace{\nabla v \cdot d\mathbf{r}}_{dv} = -dq \int_{-}^{+} dv = -vdq$$

and the work done by us is the negative of (or against) the work done by the field

$$dW_{\text{us}} = -dW_{\text{field}} = vdq$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}}$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}} = \int_0^Q v dq$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}} = \int_0^Q v dq = \int_0^Q \frac{q}{C} dq$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}} = \int_0^Q v dq = \int_0^Q \frac{q}{C} dq$$

We learned that C is constant for a certain capacitor so

$$W_{\text{us}} = \frac{1}{C} \int_0^Q q dq$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}} = \int_0^Q v dq = \int_0^Q \frac{q}{C} dq$$

We learned that C is constant for a certain capacitor so

$$W_{\text{us}} = \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \left[\frac{1}{2} q^2 \right]_0^Q$$

Energy Stored in a Capacitor

But since $C = \frac{q}{v}$ (as we saw in the previous slide) we have

$$W_{\text{us}} = \int dW_{\text{us}} = \int_0^Q v dq = \int_0^Q \frac{q}{C} dq$$

We learned that C is constant for a certain capacitor so

$$W_{\text{us}} = \frac{1}{C} \int_0^Q q dq = \frac{1}{C} \left[\frac{1}{2} q^2 \right]_0^Q = \frac{Q^2}{2C}$$

Energy Stored in a Capacitor

So we conclude: the potential energy $U = W_{\text{us}}$ stored in the capacitor of capacitance C during its charging from 0 to Q is the work done by us and is equal to

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Energy Stored in a Capacitor

So we conclude: the potential energy $U = W_{\text{us}}$ stored in the capacitor of capacitance C during its charging from 0 to Q is the work done by us and is equal to

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Since $C = \frac{Q}{V}$ we can also write this as

$$U = \frac{Q^2}{2 \frac{Q}{V}}$$

Energy Stored in a Capacitor

So we conclude: the potential energy $U = W_{\text{us}}$ stored in the capacitor of capacitance C during its charging from 0 to Q is the work done by us and is equal to

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Since $C = \frac{Q}{V}$ we can also write this as

$$U = \frac{Q^2}{2 \frac{Q}{V}} \Rightarrow U = \frac{1}{2} QV$$

Energy Stored in a Capacitor

So we conclude: the potential energy $U = W_{\text{us}}$ stored in the capacitor of capacitance C during its charging from 0 to Q is the work done by us and is equal to

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Since $C = \frac{Q}{V}$ we can also write this as

$$U = \frac{Q^2}{2 \frac{Q}{V}} \Rightarrow U = \frac{1}{2} QV$$

or also

$$U = \frac{(CV)^2}{2C}$$

Energy Stored in a Capacitor

So we conclude: the potential energy $U = W_{\text{us}}$ stored in the capacitor of capacitance C during its charging from 0 to Q is the work done by us and is equal to

$$U = \frac{1}{2} \frac{Q^2}{C}$$

Since $C = \frac{Q}{V}$ we can also write this as

$$U = \frac{Q^2}{2 \frac{Q}{V}} \Rightarrow U = \frac{1}{2} QV$$

or also

$$U = \frac{(CV)^2}{2C} \Rightarrow U = \frac{1}{2} CV^2$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}}$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad}$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad} = \frac{\frac{1}{2}\frac{\epsilon_0 A}{d}V^2}{Ad}$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad} = \frac{\frac{1}{2}\frac{\epsilon_0 A}{d}V^2}{Ad} = \frac{1}{2}\frac{\epsilon_0 AV^2}{Ad^2}$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad} = \frac{\frac{1}{2}\frac{\epsilon_0 A}{d}V^2}{Ad} = \frac{1}{2}\frac{\epsilon_0 AV^2}{Ad^2} = \frac{1}{2}\epsilon_0 \left(\frac{V}{d}\right)^2$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad} = \frac{\frac{1}{2}\frac{\epsilon_0 A}{d}V^2}{Ad} = \frac{1}{2}\frac{\epsilon_0 AV^2}{Ad^2} = \frac{1}{2}\epsilon_0 \left(\frac{V}{d}\right)^2$$

or since in parallel plate capacitor $V = Ed$

$$u = \frac{1}{2}\epsilon_0 E^2$$

Energy Density of the Capacitor's Field

We can think of the energy U as being stored in the field in the region between the plates

The associated **energy density** is the **energy per unit volume** of a capacitor with plate area A and plate separation d ,

$$u = \frac{U}{\mathcal{V}} = \frac{\frac{1}{2}CV^2}{Ad} = \frac{\frac{1}{2}\frac{\epsilon_0 A}{d}V^2}{Ad} = \frac{1}{2}\frac{\epsilon_0 AV^2}{Ad^2} = \frac{1}{2}\epsilon_0 \left(\frac{V}{d}\right)^2$$

or since in parallel plate capacitor $V = Ed$

$$u = \frac{1}{2}\epsilon_0 E^2$$

Although we have derived this relationship for a parallel-plate capacitor only, it turns out to be **valid for any capacitor in vacuum** and indeed **for any electric-field configuration in vacuum**, even if there is no capacitor there.