

PHYS 230 - Electricity and Magnetism

Lecture 26

Instructor: Saeed Rastgoo



**UNIVERSITY
OF ALBERTA**

Outline

6 Direct-Current Circuits

- Kirchhoff's Rules
- $R - C$ Circuits

All figures in these slides are from one of the following sources, unless cited otherwise:

University Physics With Modern Physics, Young & Freedman

Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett

Outline

6 Direct-Current Circuits

- Kirchhoff's Rules
- $R - C$ Circuits

All figures in these slides are from one of the following sources, unless cited otherwise:

University Physics With Modern Physics, Young & Freedman


Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett

Exercise 1


<https://epoll.srv.ualberta.ca> – Code: MBD

Figure shows a “bridge” circuit. Find the current in each resistor and the equivalent resistance of the network of five resistors.

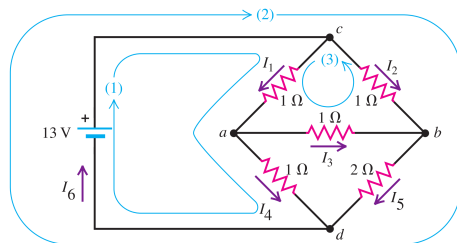


Exercise I

<https://epoll.srv.ualberta.ca> – Code: MBD

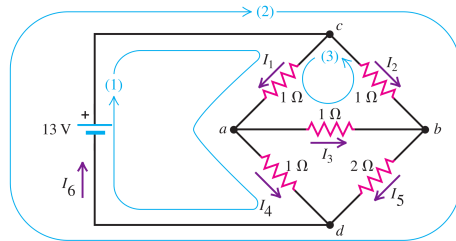


Exercise I

<https://epoll.srv.ualberta.ca> – Code: MBD

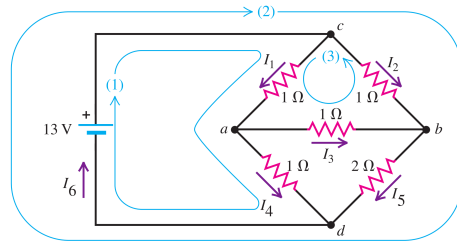

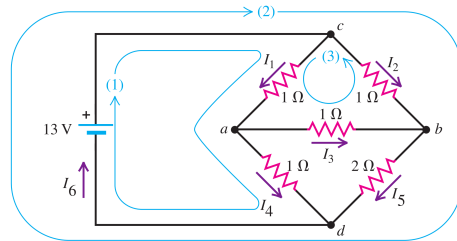Exercise I

<https://epoll.srv.ualberta.ca> – Code: MBD



Outline

6 Direct-Current Circuits

- Kirchhoff's Rules
- $R - C$ Circuits

All figures in these slides are from one of the following sources, unless cited otherwise:

University Physics With Modern Physics, Young & Freedman


Physics for Scientists and Engineers, Hawkes, et al.

Physics for Scientists and Engineers With Modern Physics, Serway, Jewett


$R - C$ Circuits: Charging Capacitors

A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit

(a) Capacitor initially uncharged

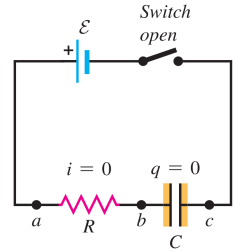


(b) Charging the capacitor

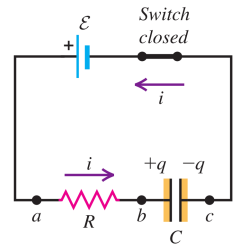


$R - C$ Circuits: Charging Capacitors

A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit. Initially the switch is open.

(a) Capacitor initially uncharged

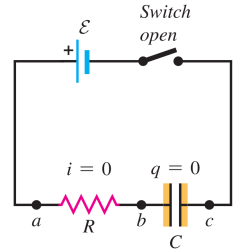

(b) Charging the capacitor

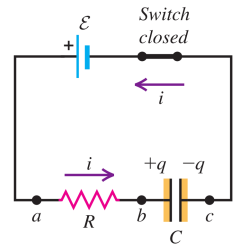


$R - C$ Circuits: Charging Capacitors


A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit

Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor

(a) Capacitor initially uncharged

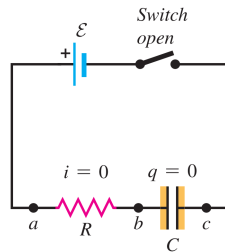

(b) Charging the capacitor

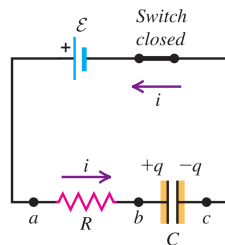


$R - C$ Circuits: Charging Capacitors

A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit


Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor

Exactly at $t = 0$, when switch closes capacitor's charge is still $q_0 = 0$

(a) Capacitor initially uncharged

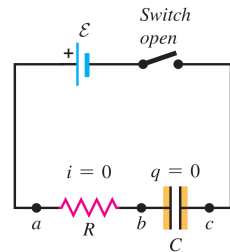

(b) Charging the capacitor

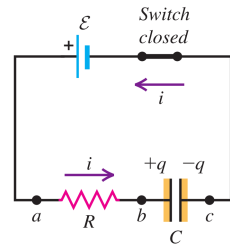

$R - C$ Circuits: Charging Capacitors


A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit

Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor


Exactly at $t = 0$, when switch closes capacitor's charge is still $q_0 = 0$; using Kirchhoff's loop rule we get

$$v_a - I_0 R - \frac{q_0}{v_{cb}} + \mathcal{E} = v_a$$

(a) Capacitor initially uncharged

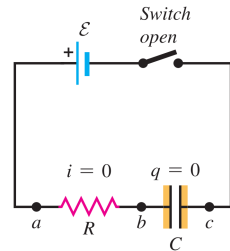

(b) Charging the capacitor

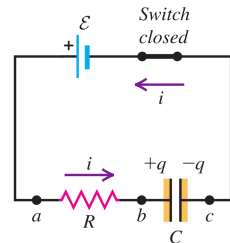

$R - C$ Circuits: Charging Capacitors


A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit

Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor


Exactly at $t = 0$, when switch closes capacitor's charge is still $q_0 = 0$; using Kirchhoff's loop rule we get

$$v_a - I_0 R - \frac{q_0}{v_{cb}} + \mathcal{E} = v_a \Rightarrow I_0 = \frac{\mathcal{E}}{R}$$

(a) Capacitor initially uncharged

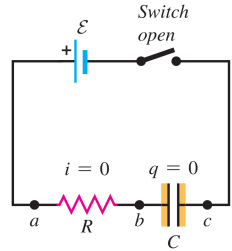

(b) Charging the capacitor

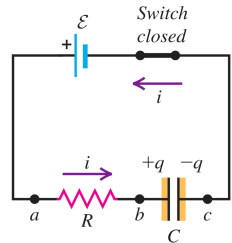

$R - C$ Circuits: Charging Capacitors

A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit


Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor

Exactly at $t = 0$, when switch closes capacitor's charge is still $q_0 = 0$; using Kirchhoff's loop rule we get


$$v_a - I_0 R - \frac{q_0}{v_{cb}} + \mathcal{E} = v_a \Rightarrow I_0 = \frac{\mathcal{E}}{R}$$

As the capacitor charges, v_{cb} increases, and since $v_{ba} + v_{cb} = \mathcal{E}$, V_{ba} decreases due to a decrease in current.

(a) Capacitor initially uncharged

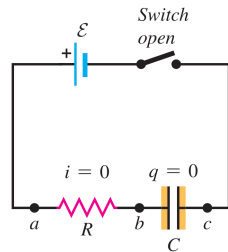

(b) Charging the capacitor

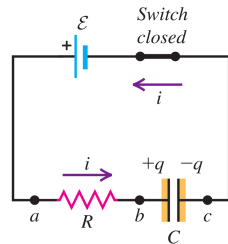

$R - C$ Circuits: Charging Capacitors

A circuit with a battery, a resistance and a capacitor is called an $R - C$ circuit

Initially the switch is open. At $t = 0$, we close the switch, current around the loop begins charging the capacitor

Exactly at $t = 0$, when switch closes capacitor's charge is still $q_0 = 0$; using Kirchhoff's loop rule we get


$$v_a - I_0 R - \frac{q_0}{v_{cb}} + \mathcal{E} = v_a \Rightarrow I_0 = \frac{\mathcal{E}}{R}$$

As the capacitor charges, v_{cb} increases, and since $v_{ba} + v_{cb} = \mathcal{E}$, V_{ba} decreases due to a decrease in current.


After a long time the capacitor is fully charged, $I \rightarrow 0$, and $v_{ba} \rightarrow 0$.

Then $v_{cb} = \mathcal{E}$.

(a) Capacitor initially uncharged

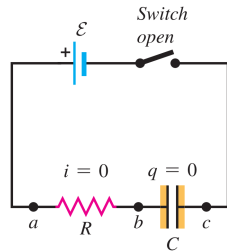


(b) Charging the capacitor

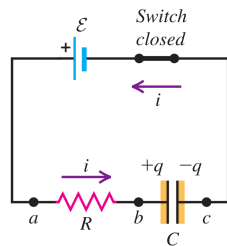


$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit

(a) Capacitor initially uncharged

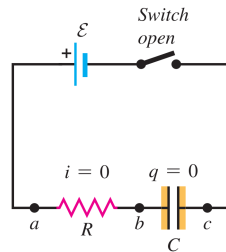

(b) Charging the capacitor

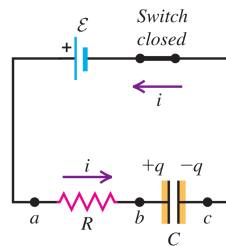


$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit


The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$

(a) Capacitor initially uncharged

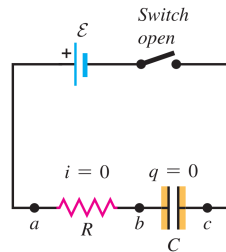

(b) Charging the capacitor

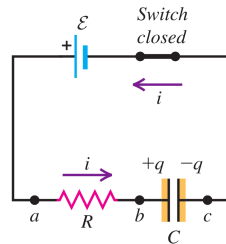

$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit


The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0$$

(a) Capacitor initially uncharged

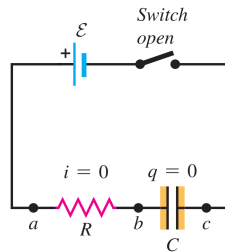

(b) Charging the capacitor

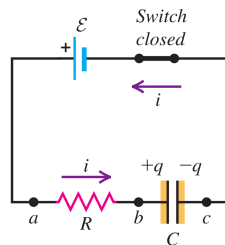

$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit


The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

(a) Capacitor initially uncharged

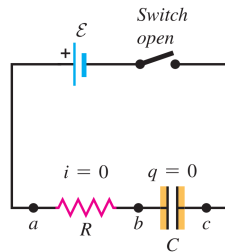

(b) Charging the capacitor

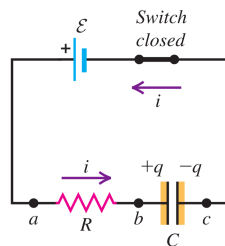

$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit


The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

(a) Capacitor initially uncharged

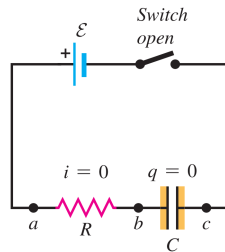

(b) Charging the capacitor

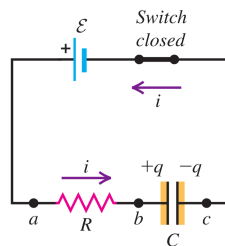

$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit


The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = -\frac{1}{RC} (q - C\mathcal{E})$$

(a) Capacitor initially uncharged

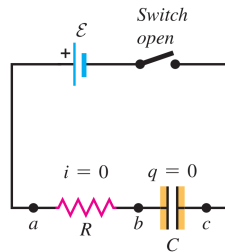

(b) Charging the capacitor

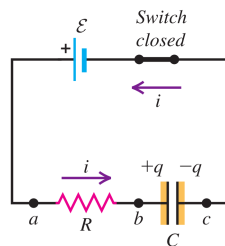

R – C Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit

The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = -\frac{1}{RC} (q - C\mathcal{E})$$


Rearranging this equation we get

$$\frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} dt$$

(a) Capacitor initially uncharged

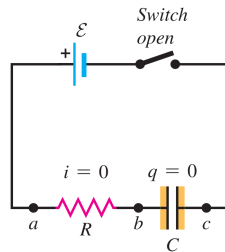

(b) Charging the capacitor

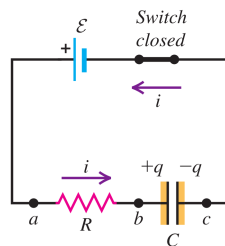

$R - C$ Circuits: Charging Capacitors

At $t > 0$, but before the capacitor is fully charged, let q represent the charge on the capacitor and i the current in the circuit

The instantaneous potential differences v_{ba} and v_{cb} are

$$v_{ba} = iR, \quad v_{cb} = \frac{q}{C}$$


Using these in Kirchhoff's loop rule,

$$\mathcal{E} - iR - \frac{q}{C} = 0 \Rightarrow i = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} \Rightarrow \frac{dq}{dt} = -\frac{1}{RC} (q - C\mathcal{E})$$


Rearranging this equation we get

$$\frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} dt \Rightarrow \int_0^q \frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} \int_0^t dt$$

(a) Capacitor initially uncharged

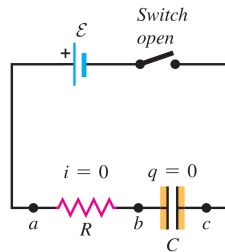

(b) Charging the capacitor

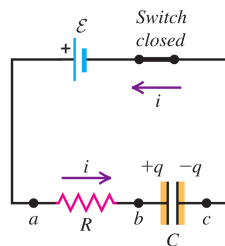


$R - C$ Circuits: Charging Capacitors


We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC}$$

(a) Capacitor initially uncharged

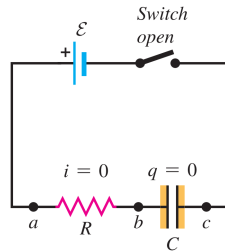

(b) Charging the capacitor

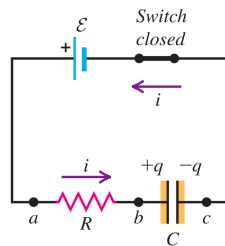


$R - C$ Circuits: Charging Capacitors


We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC} \Rightarrow \ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = -\frac{t}{RC}$$

(a) Capacitor initially uncharged

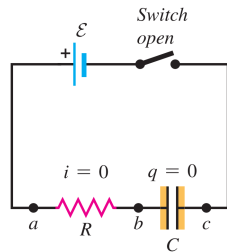

(b) Charging the capacitor

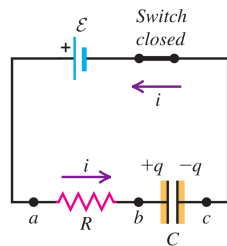


$R - C$ Circuits: Charging Capacitors


We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC} \Rightarrow \ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC}$$

(a) Capacitor initially uncharged

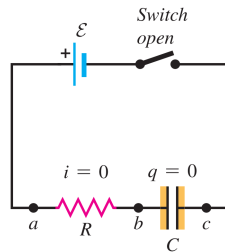

(b) Charging the capacitor

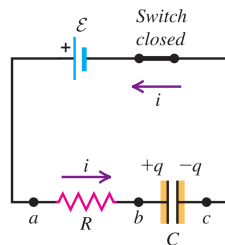

$R - C$ Circuits: Charging Capacitors


We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC} \Rightarrow \ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC}$$


And exponentiating both sides we get

$$q = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}}\right)$$

(a) Capacitor initially uncharged

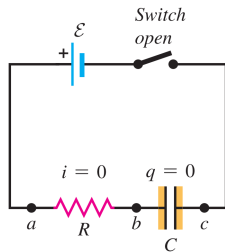

(b) Charging the capacitor

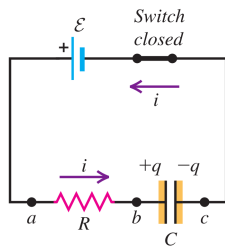

R – C Circuits: Charging Capacitors

We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC} \Rightarrow \ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC}$$


And exponentiating both sides we get

$$q = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}}\right)$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = C\mathcal{E} \left(1 - e^{-\frac{\infty}{RC}}\right) \Rightarrow Q_f = C\mathcal{E}$$

(a) Capacitor initially uncharged

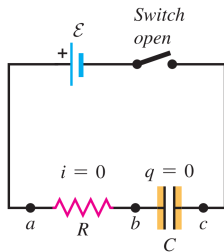

(b) Charging the capacitor

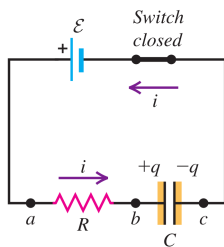

R – C Circuits: Charging Capacitors

We can solve this integral using substitution $u = q - C\mathcal{E} \Rightarrow du = dq$, where the integral limits change to $-C\mathcal{E}$ to $q - C\mathcal{E}$

$$[\ln(u)]_{-C\mathcal{E}}^{q-C\mathcal{E}} = -\frac{t}{RC} \Rightarrow \ln(q - C\mathcal{E}) - \ln(-C\mathcal{E}) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC}$$

And exponentiating both sides we get

$$q = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}}\right)$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = C\mathcal{E} \left(1 - e^{-\frac{\infty}{RC}}\right) \Rightarrow Q_f = C\mathcal{E}$$


So we can write the charging equation

$$q = Q_f \left(1 - e^{-\frac{t}{RC}}\right)$$

(a) Capacitor initially uncharged

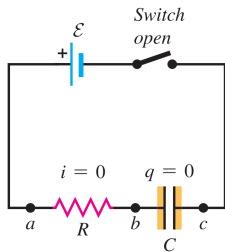

(b) Charging the capacitor

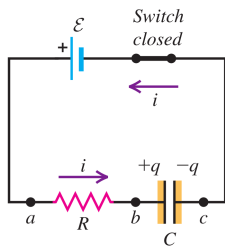


$R - C$ Circuits: Charging Capacitors


Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right)$$

(a) Capacitor initially uncharged

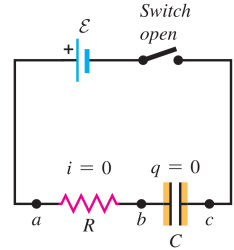

(b) Charging the capacitor

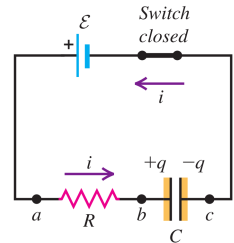


$R - C$ Circuits: Charging Capacitors


Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right) \Rightarrow i = \frac{C\mathcal{E}}{RC} e^{-\frac{t}{RC}}$$

(a) Capacitor initially uncharged

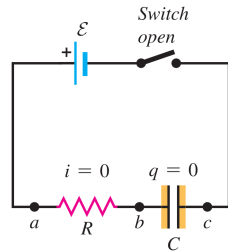

(b) Charging the capacitor

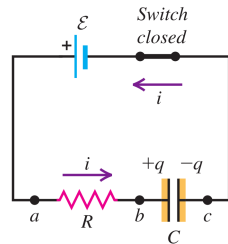


$R - C$ Circuits: Charging Capacitors


Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right) \Rightarrow i = \frac{C\mathcal{E}}{RC} e^{-\frac{t}{RC}} \Rightarrow \boxed{i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}}$$

(a) Capacitor initially uncharged

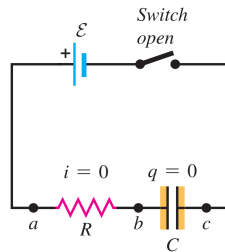

(b) Charging the capacitor

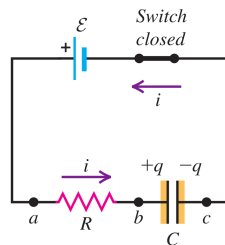


$R - C$ Circuits: Charging Capacitors


Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right) \Rightarrow i = \frac{C\mathcal{E}}{RC} e^{-\frac{t}{RC}} \Rightarrow \boxed{i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}} \Rightarrow \boxed{i = I_0 e^{-\frac{t}{RC}}}$$

(a) Capacitor initially uncharged

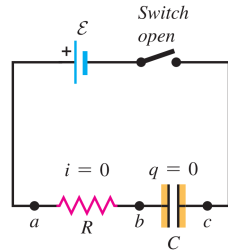

(b) Charging the capacitor

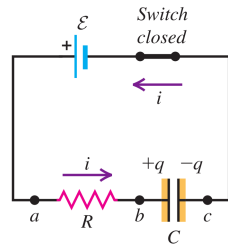

R – C Circuits: Charging Capacitors


Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right) \Rightarrow i = \frac{C\mathcal{E}}{RC} e^{-\frac{t}{RC}} \Rightarrow \boxed{i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}} \Rightarrow \boxed{i = I_0 e^{-\frac{t}{RC}}}$$


When $t = RC$, we get

$$q = C\mathcal{E} (1 - e^{-1}) = C\mathcal{E} \left(1 - \frac{1}{e} \right) = 0.632C\mathcal{E} = 0.632Q_f$$

(a) Capacitor initially uncharged

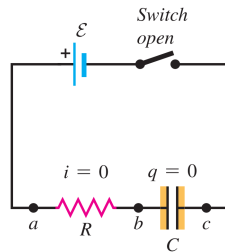

(b) Charging the capacitor

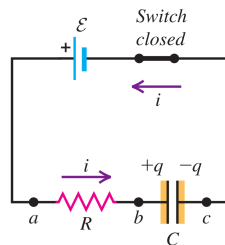

R – C Circuits: Charging Capacitors

Taking derivative of both sides w.r.t. t

$$\frac{dq}{dt} = C\mathcal{E} \left(-\frac{d}{dt} e^{-\frac{t}{RC}} \right) \Rightarrow i = \frac{C\mathcal{E}}{RC} e^{-\frac{t}{RC}} \Rightarrow \boxed{i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}} \Rightarrow \boxed{i = I_0 e^{-\frac{t}{RC}}}$$


When $t = RC$, we get

$$q = C\mathcal{E} (1 - e^{-1}) = C\mathcal{E} \left(1 - \frac{1}{e} \right) = 0.632C\mathcal{E} = 0.632Q_f$$


The **time constant** or the **relaxation time** τ of the circuit is defined as the time after the charge/current in the $R - C$ circuit reaches 0.632 its final value

$$\boxed{\tau = RC}$$

(a) Capacitor initially uncharged

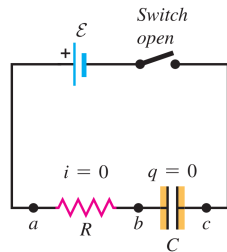


(b) Charging the capacitor

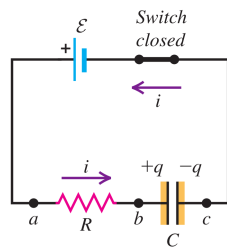


$R - C$ Circuits: Discharging Capacitors

Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

(a) Capacitor initially charged

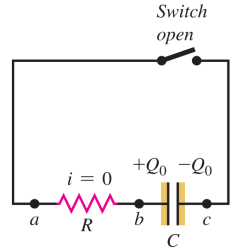

(b) Discharging the capacitor

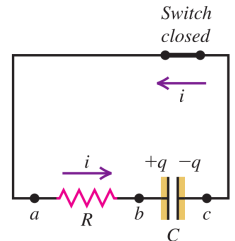


$R - C$ Circuits: Discharging Capacitors


Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.

(a) Capacitor initially charged

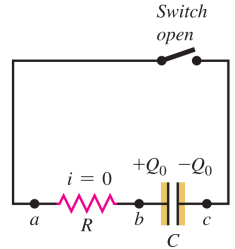

(b) Discharging the capacitor

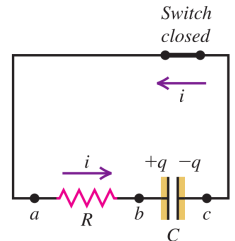

$R - C$ Circuits: Discharging Capacitors


Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.


During discharge, using Kirchhoff's loop rule we get

$$V_a - iR - \frac{q}{C} = V_a$$

(a) Capacitor initially charged

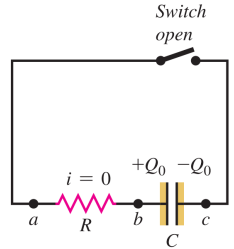

(b) Discharging the capacitor

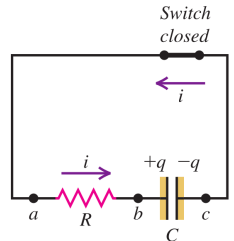

R – C Circuits: Discharging Capacitors


Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.


During discharge, using Kirchhoff's loop rule we get

$$V_a - iR - \frac{q}{C} = V_a \Rightarrow i = -\frac{1}{RC}q$$

(a) Capacitor initially charged

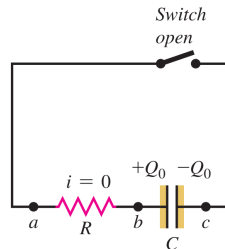

(b) Discharging the capacitor

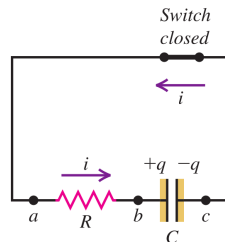

R – C Circuits: Discharging Capacitors


Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.


During discharge, using Kirchhoff's loop rule we get

$$V_a - iR - \frac{q}{C} = V_a \Rightarrow i = -\frac{1}{RC}q \Rightarrow \frac{dq}{dt} = -\frac{1}{RC}q$$

(a) Capacitor initially charged

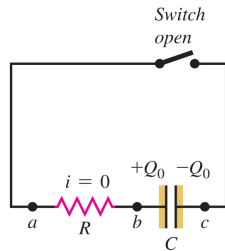

(b) Discharging the capacitor

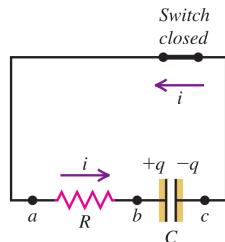

R – C Circuits: Discharging Capacitors

Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.


During discharge, using Kirchhoff's loop rule we get

$$V_a - iR - \frac{q}{C} = V_a \Rightarrow i = -\frac{1}{RC}q \Rightarrow \frac{dq}{dt} = -\frac{1}{RC}q$$


Rearranging this equation we get

$$\frac{dq}{q} = -\frac{1}{RC}dt$$

(a) Capacitor initially charged

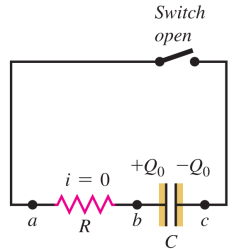

(b) Discharging the capacitor

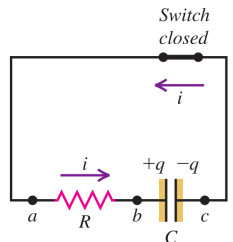

R – C Circuits: Discharging Capacitors

Now we remove the battery, replace it with an open switch, reset our time, and close the switch; at this time $q = Q_0$

The capacitor then discharges through the resistor, and its charge eventually decreases to zero.


During discharge, using Kirchhoff's loop rule we get

$$V_a - iR - \frac{q}{C} = V_a \Rightarrow i = -\frac{1}{RC}q \Rightarrow \frac{dq}{dt} = -\frac{1}{RC}q$$


Rearranging this equation we get

$$\frac{dq}{q} = -\frac{1}{RC}dt \Rightarrow \int_{Q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$

(a) Capacitor initially charged

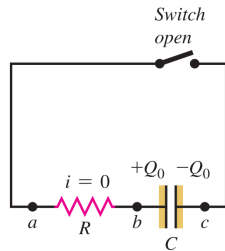

(b) Discharging the capacitor

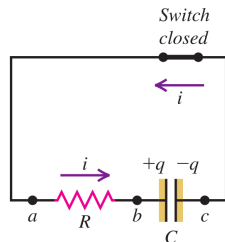


$R - C$ Circuits: Discharging Capacitors


We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC}$$

(a) Capacitor initially charged

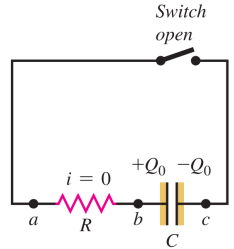

(b) Discharging the capacitor

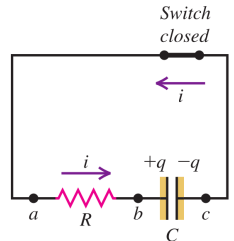


$R - C$ Circuits: Discharging Capacitors


We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC}$$

(a) Capacitor initially charged

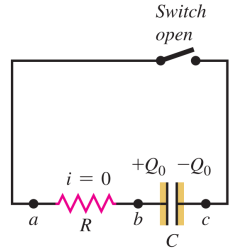

(b) Discharging the capacitor

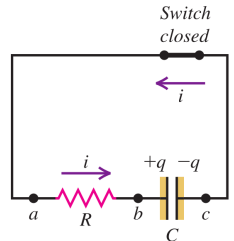


$R - C$ Circuits: Discharging Capacitors


We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$

(a) Capacitor initially charged

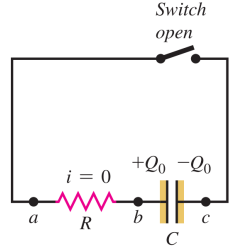

(b) Discharging the capacitor

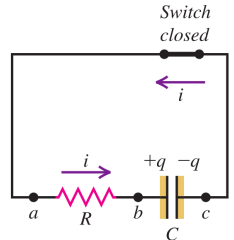

$R - C$ Circuits: Discharging Capacitors


We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$


And exponentiating both sides we get

$$q = Q_0 e^{-\frac{t}{RC}}$$

(a) Capacitor initially charged

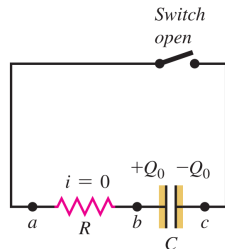

(b) Discharging the capacitor

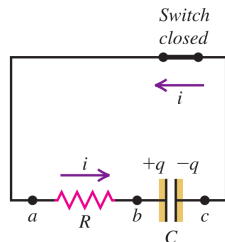

R – C Circuits: Discharging Capacitors

We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$


And exponentiating both sides we get

$$q = Q_0 e^{-\frac{t}{RC}}$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = 0$$

(a) Capacitor initially charged

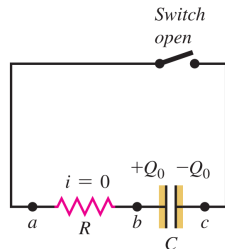

(b) Discharging the capacitor

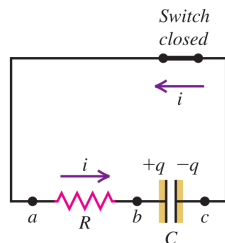

R – C Circuits: Discharging Capacitors

We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$

And exponentiating both sides we get

$$q = Q_0 e^{-\frac{t}{RC}}$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = 0$$


Taking the time derivative of both sides yields the current equation

$$\frac{dq}{dt} = Q_0 \frac{d}{dt} e^{-\frac{t}{RC}}$$

(a) Capacitor initially charged

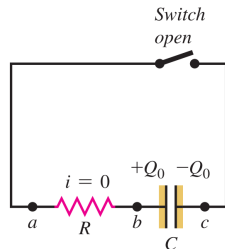

(b) Discharging the capacitor

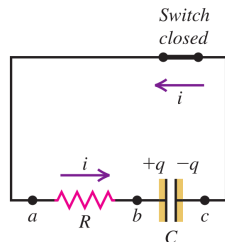

R – C Circuits: Discharging Capacitors

We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$

And exponentiating both sides we get

$$q = Q_0 e^{-\frac{t}{RC}}$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = 0$$


Taking the time derivative of both sides yields the current equation

$$\frac{dq}{dt} = Q_0 \frac{d}{dt} e^{-\frac{t}{RC}} \Rightarrow i = -\frac{Q_0}{RC} e^{-\frac{t}{RC}}$$

(a) Capacitor initially charged

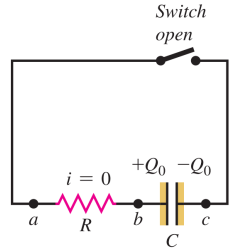

(b) Discharging the capacitor

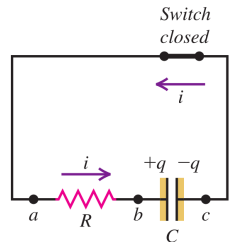

R – C Circuits: Discharging Capacitors

We can solve this integral as

$$[\ln(q)]_{Q_0}^q = -\frac{t}{RC} \Rightarrow \ln(q) - \ln(Q_0) = -\frac{t}{RC} \Rightarrow \ln\left(\frac{q}{Q_0}\right) = -\frac{t}{RC}$$

And exponentiating both sides we get

$$q = Q_0 e^{-\frac{t}{RC}}$$


When a long time passes $t \rightarrow \infty$ we get the full charge

$$Q_f = 0$$

Taking the time derivative of both sides yields the current equation

$$\frac{dq}{dt} = Q_0 \frac{d}{dt} e^{-\frac{t}{RC}} \Rightarrow i = -\frac{Q_0}{RC} e^{-\frac{t}{RC}} \Rightarrow i = -I_0 e^{-\frac{t}{RC}}$$

(a) Capacitor initially charged

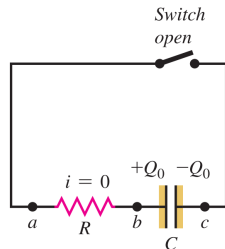

(b) Discharging the capacitor

